

Digital Circuit Design — Lab 02


A. Design of Carry Lookahead Adder, CLA, and Borrow Lookahead Subtractor, BLS

a. Carry Lookahead generator

 (i) Gate-level modeling

```
~/Documents/GitHub/Digital-Circuit-Design/Lab2 iverilog -o test Lab2_CLG_gate.v t_Lab2_CLG.v
~/Documents/GitHub/Digital-Circuit-Design/Lab2 vvp test
```


```
1 1 0 1
1 0 0 0
1 1 0 1
1 1 0 0
0 1 0 1
1 0 1 1
```



 (ii) Dataflow modeling

```
~/Documents/GitHub/Digital-Circuit-Design/Lab2 iverilog -o test Lab2_CLG_dataflow.v t_Lab2_CLG.v
~/Documents/GitHub/Digital-Circuit-Design/Lab2 vvp test
```

```
1 1 0 1
1 0 0 0
1 1 0 1
1 1 0 0
0 1 0 1
1 0 1 1
```




(iii) Behavior modeling

```

~/Documents/GitHub/Digital-Circuit-Design/Lab2 iverilog -o test Lab2_CLG_behavior.v t_Lab2_CLG.v
~/Documents/GitHub/Digital-Circuit-Design/Lab2 vvp test
1 1 0 1
1 0 0 0
1 1 0 1
1 1 0 0
0 1 0 1
1 0 1 1

```

 


此三種設計電路的方法測試結果正確且波形圖完全相同。第四項的推法而可以藉由前三項找出規律，即為前一項的每一項去 **and** $P(i-1)$ ，所以說，我們可以得到以下式子：

$$C1 = P0C0 \oplus G0$$

$$C2 = P1P0C0 \oplus P1G0 \oplus G1$$


$$C3 = P2P1P0C0 \oplus P2P1G0 \oplus P2G1 \oplus G2$$
 
$$\rightarrow C4 = P3P2P1P0C0 \oplus P3P2P1G0 \oplus P3P2G1 \oplus P3G2 \oplus G3$$



 b. Carry Lookahead Adder

```
~/Documents/GitHub/Digital-Circuit-Design/Lab2 iverilog -o test Lab2_4_bit_CLA.v t_Lab2_4_b
it_CLA.v Lab2_CLG_behavior.v
~/Documents/GitHub/Digital-Circuit-Design/Lab2 vvp test 13:25:19
VCD info: dumpfile Lab2_4_bit_CLA.vcd opened for output.
C Sum
1 0010
1 0101
1 0010
1 0101
0 1010
1 0111
1 1111
1 0000
```



這題藉由上題的 **Carry Lookahead generator** 去產生每位的 **carry**，然後再藉由傳進去前算好的 **Pi**，得到 **Si**。


$$P_i = A_i \oplus B_i$$

$$G_i = A_i \& B_i$$

$$\rightarrow S_i = C_i \oplus P_i$$

 B. 4-bit Borrow Lookahead Subtractor, BLS

```
~/Documents/GitHub/Digital-Circuit-Design/Lab2 iverilog -o test Lab2_4_bit_BLS.v t_Lab2_4_bi
t_BLS.v Lab2_CLG_behavior.v
~/Documents/GitHub/Digital-Circuit-Design/Lab2 vvp test 12:21:19
VCD info: dumpfile Lab2_4_bit_BLS.vcd opened for output.
B Dif
0 1000
0 0011
1 1000
1 1011
0 0000
1 1111
1 0001
1 0000
```



這題比較特別，因為要在不在 **CLG** 做任何改變而成為 **BLG**，所以我先觀察作業 27 題的算式如下：

$$P_i = X_i \oplus Y_i$$

$$G_i = \sim X_i \& Y_i$$

$$D_i = P_i \oplus B_i$$

$$B_{i+1} = G_i + \sim P_i B_i$$

這樣不能直接使用 CLG，因為在 B_{i+1} 裡面 P_i 多了一個 not，所以我將 BLS 的 P_i 做了一點改變，如下：

$$P_i = \sim(X_i \oplus Y_i)$$

$$G_i = \sim X_i \& Y_i$$

所以 D_i 與 B_i 就成了：


$$D_i = \sim P_i \oplus B_i$$

$$B_{i+1} = G_i + P_i B_i$$

這樣 B_i 也就成了與 C_i 相同的格式，所以可以直接使用 CLG 產生 BLG。

 C. Excess-3 Adder

```
~/Documents/GitHub/Digital-Circuit-Design/Lab2 iverilog -o test Lab2_Excess_3_adder_behavior
.v t_Lab2_Excess_3_adder_behavior.v Lab2_4_bit_CLA.v Lab2_CLG_behavior.v
~/Documents/GitHub/Digital-Circuit-Design/Lab2 vvp test 12:44:10
VCD info: dumpfile Lab2_Excess_3_adder_behavior.vcd opened for output.
C Sum
0 0011
0 0100
0 1100
1 0011
1 1011
1 1100
```



運用前題的 CLA 將輸入 A B 相加，再藉由 CLA 產生的 Carry 去判斷要加上 4'b0011 還是減去 4'b0011，細節參考作業 28 題。

D. Conclusion

這次是第二次要用到 Verilog 的功課，明顯比上一次難許多。其中一點點的錯誤編譯器並不會找出來，而是要自己去找到，所以我一開始的 CLG 中一直產生不出我想要的輸出，導致花了超多時間去找不對的方向，結果只是 C0 寫成 C[0] 這種明顯的錯誤。但藉由這次終於有點感覺 Verilog 的語法與怎麼實作一個電路。